



EW-2 Project

SOUND AMPLIFIER

Haripraveen Subramanian 2018102031


Kartik Agarwal 2018102017



Proposed Design


- An audio amp consists of an input source(mic) with peak-to-peak input of 10-20mV.
- A pre-amp stage
- A gain stage . Multiplication of both the gains will be around 500.
- A Volume control(if possible).
- A low band-pass filter with a pass range of(20Hz-20kHz).
- A power amplifier.
- A Load of around 8 ohms, into the output.

Microphone

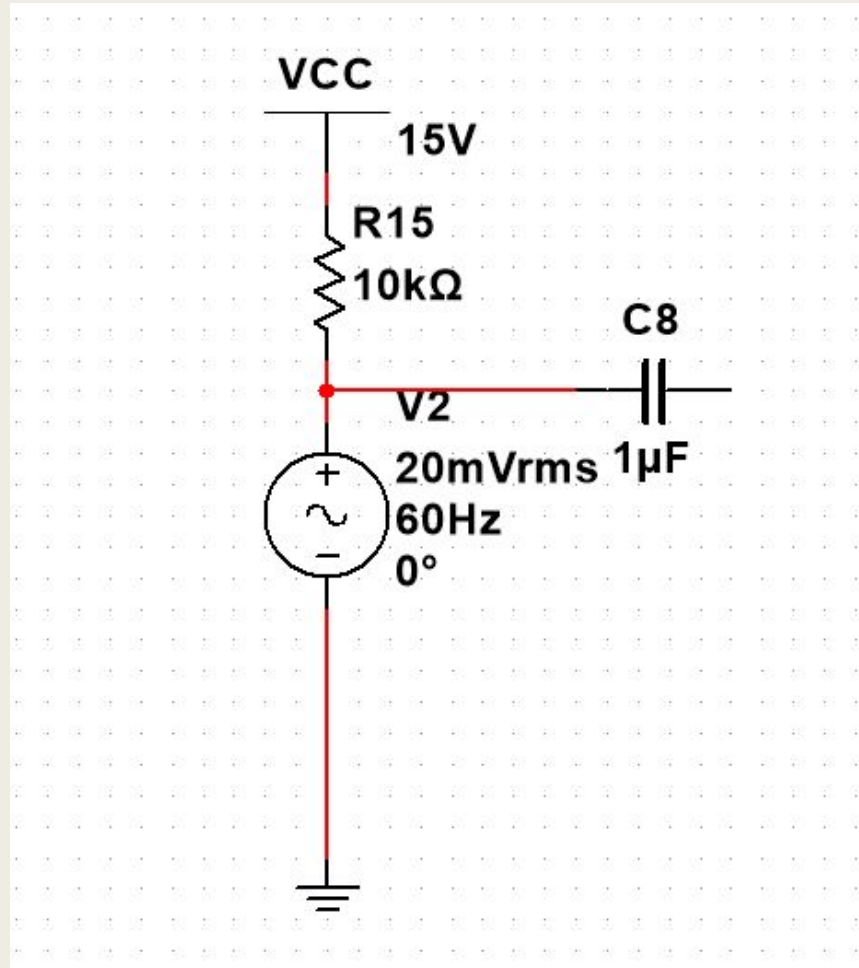

This is a standard circuit for a mic. A 10 kOhms resistor is used to control sensitivity of the mic and the capacitor is used to remove the DC component, so that only AC signal passes.


Pre-Amplifier Stage

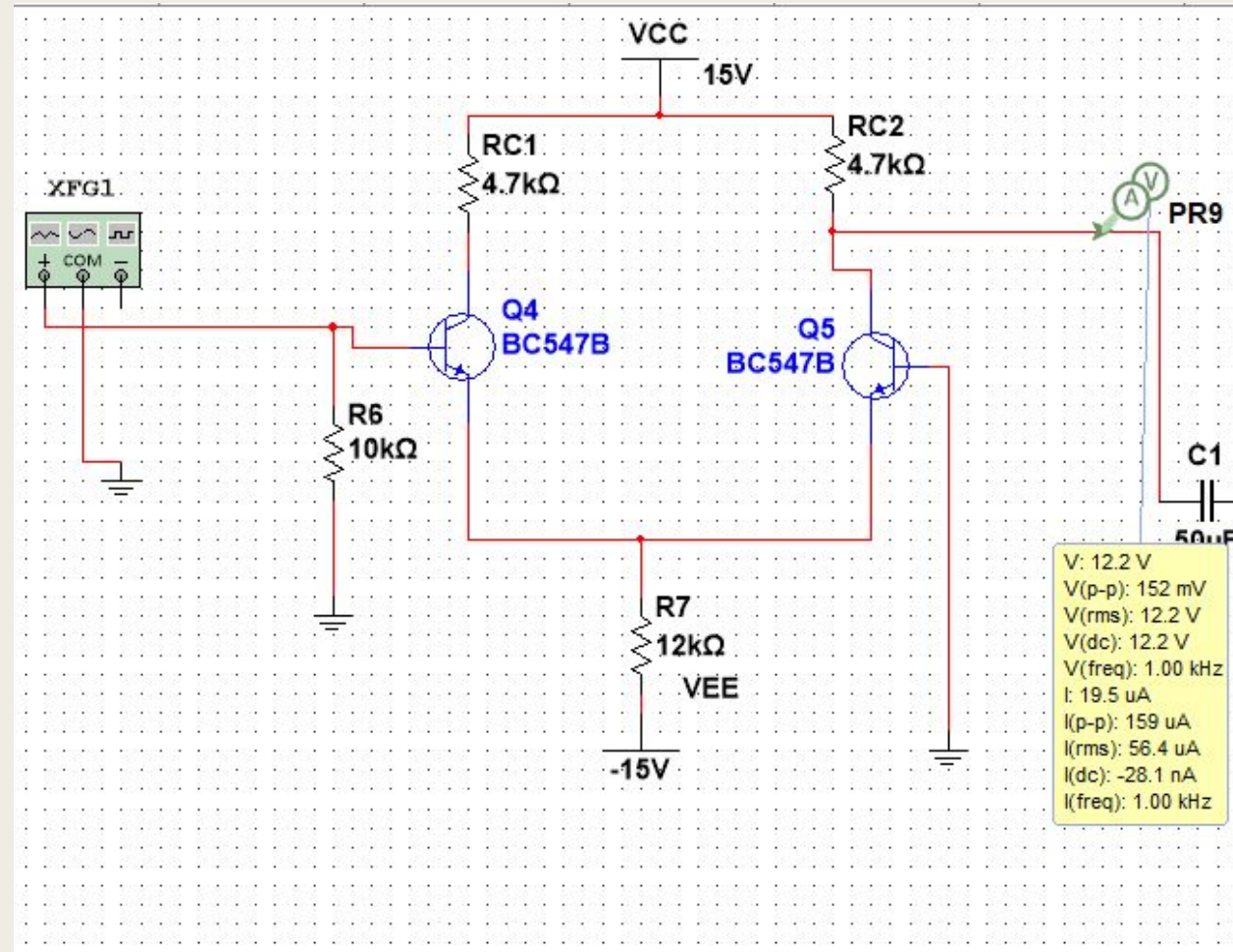

- The Pre-amp stage basically consists of a Differential amplifier as shown in the picture on the previous slide.
- Gain = 9


Gain Stage

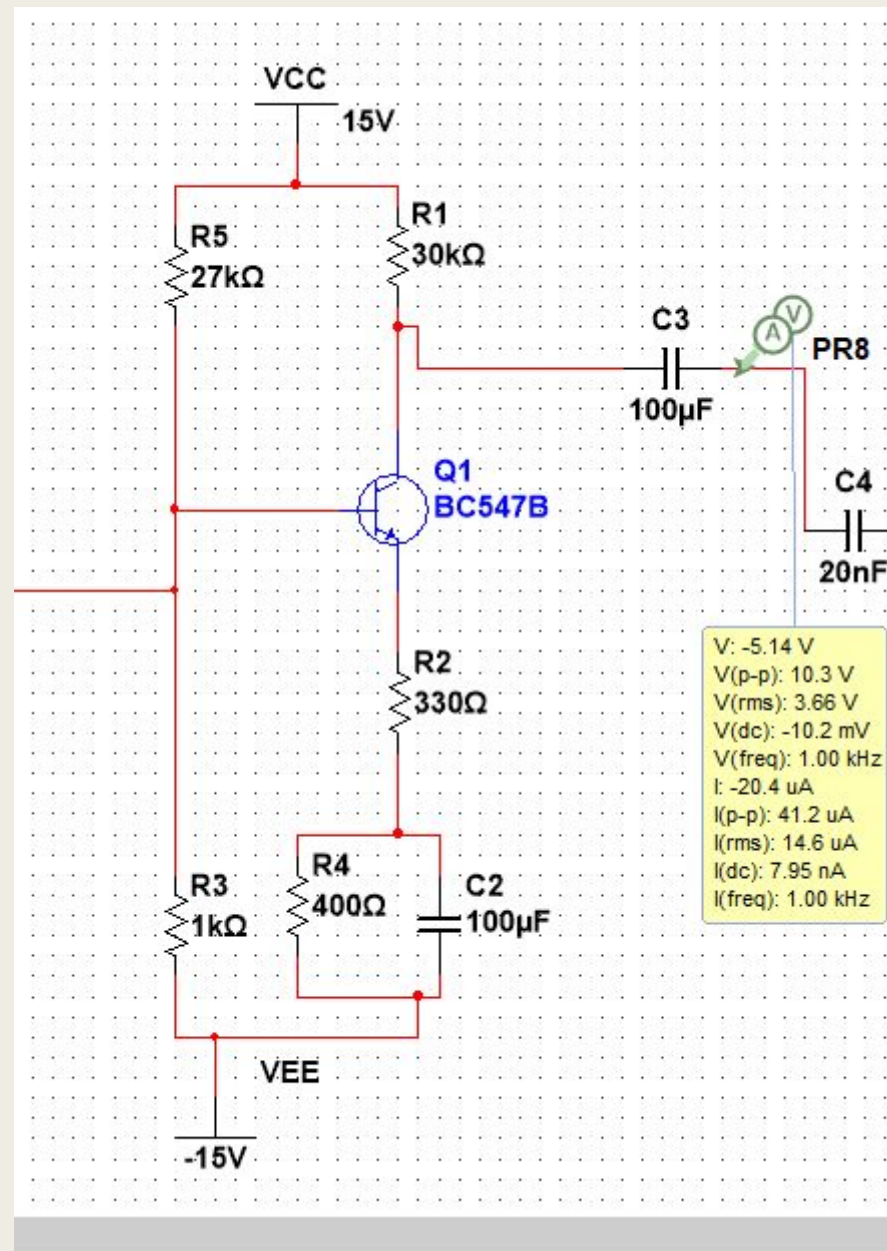
- The Gain Stage will be a BJT amplifier with which the input impedance matches with the output impedance of the Pre-amplifier stage and the output impedance matches with the input impedance of the Filter or Volume Control stage.
- Gain of common-emitter amplifier = 45



Filter

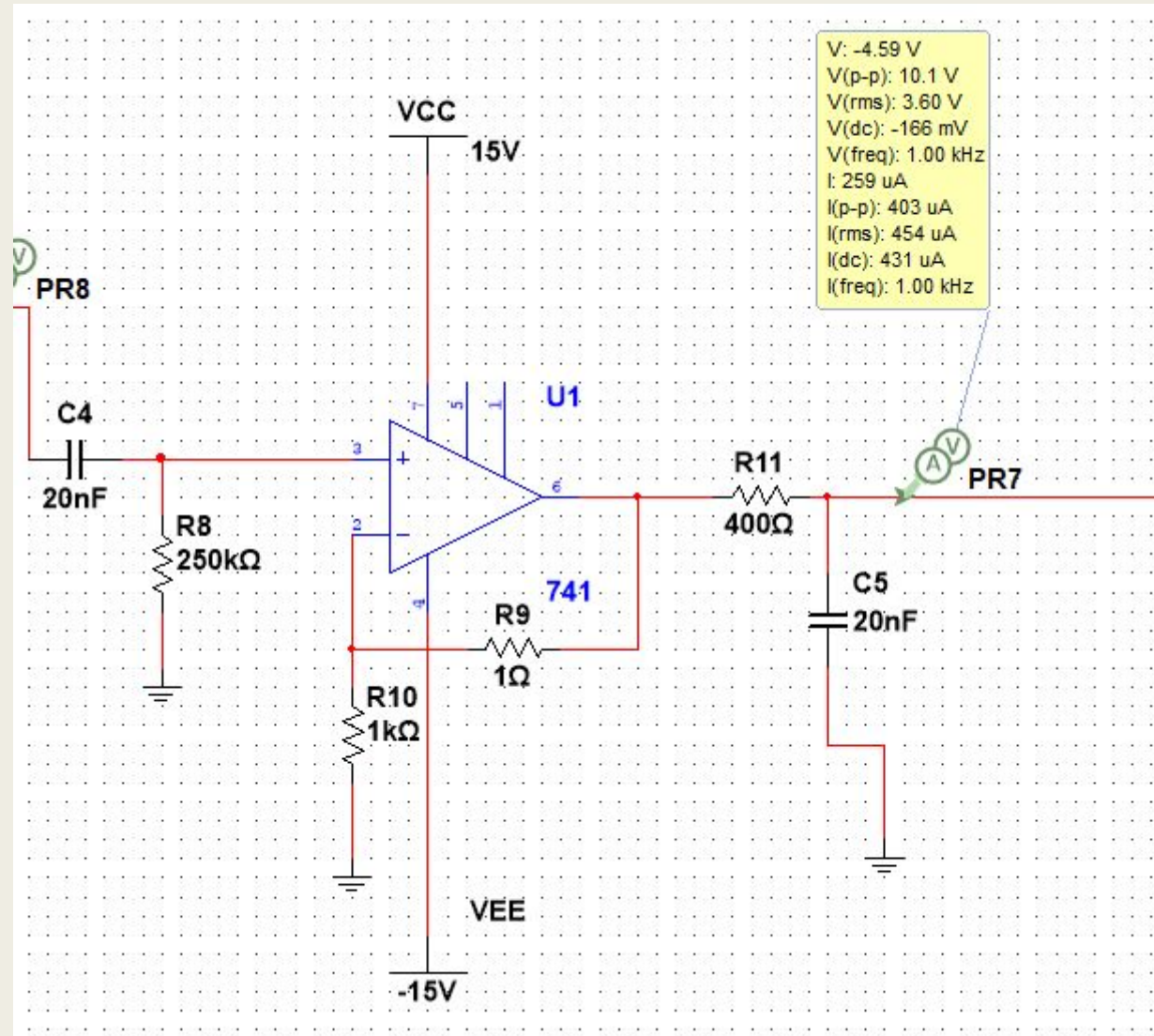- The filter will be done using a IC, IC 741, which will be designed as a low bandpass filter.
- We used an active filter with gain of 0.95
- The cutoff frequency are set at 32Hz and 19.8kHz



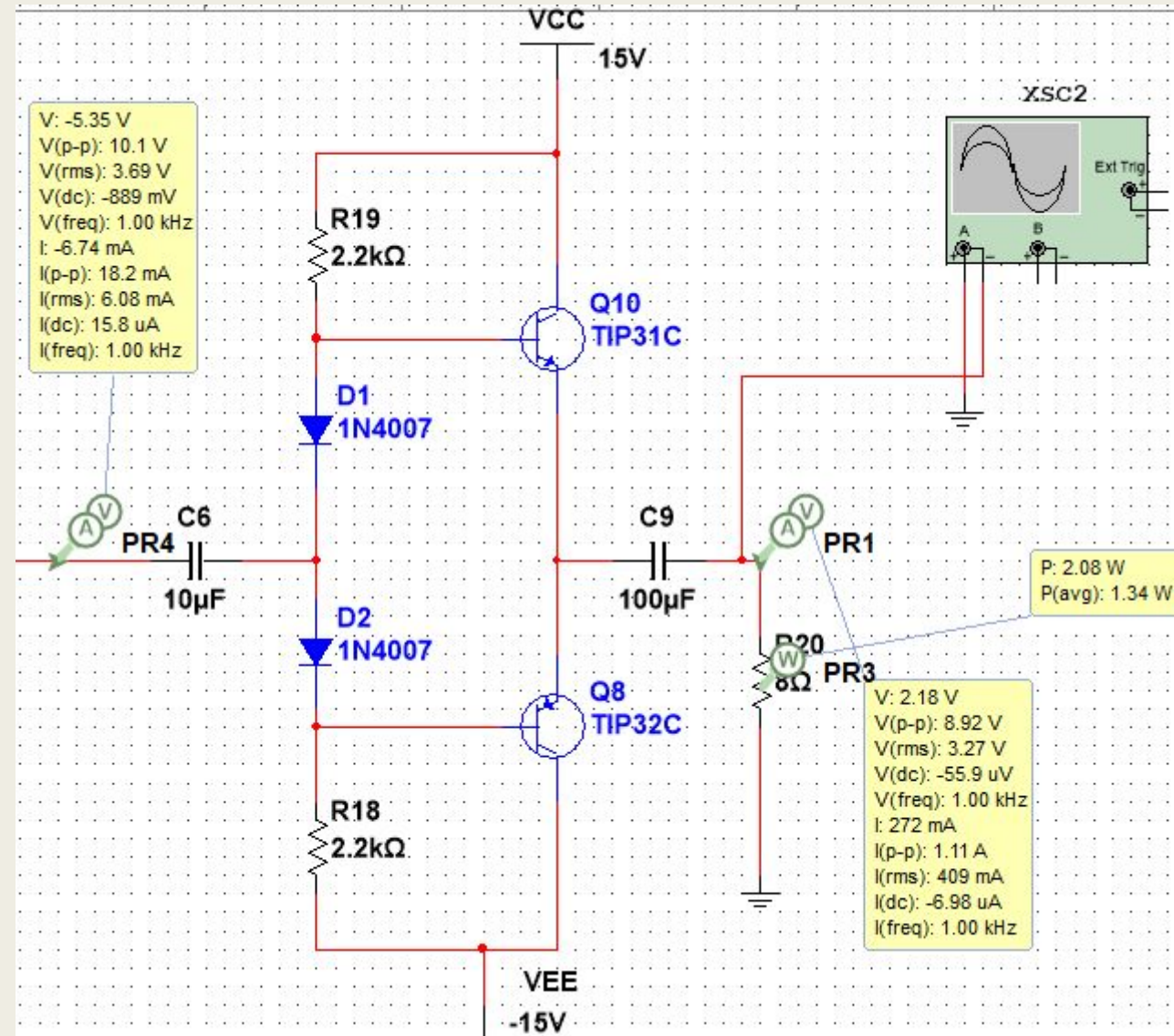

Power Amplifier

- We will be using a class AB power amplifier in our circuit as they have a sufficiently high efficiency(60%) and reduces distortion of signal near crossover region using a combination of diodes and resistors.
- Power output is 1.34W with $V_{rms} = 3.27$

Thank
You